

🔑 main ▾ [Digital-electronics-1](#) / [Labs](#) / [06-display\\_driver](#) / [README.md](#)

Go to file ...

👤 xkocum00 Update README.md

Latest commit 01530cb 15 minutes ago 🕒 History

👤 1 contributor

224 lines (196 sloc) | 8.07 KB

Raw

Blame



# Part 1: Preparation tasks


## Timing diagram figure for displaying value 3.142

```
{signal: [
  ['Digit position',
    {name: 'disp_dig_o(3)', wave: 'xx01..01..xx', },
    {name: 'disp_dig_o(2)', wave: 'xx101..01.xx', },
    {name: 'disp_dig_o(1)', wave: 'xx1.01..01xx', },
    {name: 'disp_dig_o(0)', wave: 'xx1..01..0xx', },
  ],
  ['Seven-segment data',
    {name: '4-digit value to display', wave: 'xx3333555599', data: ['3','1','4','2','3','1','4','2','3','1']},
    {name: 'A: disp_seg_o(6)', wave: 'xx01.0.1.0x.', },
    {name: 'B: disp_seg_o(5)', wave: 'xx0.....xx', },
    {name: 'C: disp_seg_o(4)', wave: 'xx0..10..1xx', },
    {name: 'D: disp_seg_o(3)', wave: 'xx01..01..xx', },
  ]
]}
```

```

{name: 'E: disp_seg_o(2)', wave: 'xx1..01..0xx', },
{name: 'F: disp_seg_o(1)', wave: 'xx1.01..01xx', },
{name: 'G: disp_seg_o(0)', wave: 'xx010..10.xx', },
],
{name: 'Decimal point: DP', wave: 'xx01..01..01'},
],
head: {
  text: '4ms 4ms 4ms 4ms 4ms 4ms 4ms 4ms',
},
}

```

 

## 2) Display driver. Submit:

## Listing of VHDL code of the process p\_mux with syntax highlighting.

---

```
p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
    case s_cnt is
        when "11" =>
            s_hex <= data3_i;
            dp_o  <= dp_i(3);
            dig_o <= "0111";

        when "10" =>
            s_hex <= data2_i;
            dp_o  <= dp_i(2);
            dig_o <= "1011";

        when "01" =>
            s_hex <= data1_i;
            dp_o  <= dp_i(1);
            dig_o <= "1101";

        when others =>
            s_hex <= data0_i;
            dp_o  <= dp_i(0);
            dig_o <= "1110";
    end case;
end process p_mux;
```

## Listing of VHDL testbench file tb\_driver\_7seg\_4digits with syntax highlighting and asserts,

---

```
library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----

entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
```

```

end entity tb_driver_7seg_4digits;

-----

-- Architecture body for testbench
-----

architecture testbench of tb_driver_7seg_4digits is

    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time      := 10 ns;

    --Local signals
    signal s_clk_100MHz : std_logic;
    --- WRITE YOUR CODE HERE
    signal s_reset      : std_logic;

    signal s_data0_i    : std_logic_vector(4 - 1 downto 0);
    signal s_data1_i    : std_logic_vector(4 - 1 downto 0);
    signal s_data2_i    : std_logic_vector(4 - 1 downto 0);
    signal s_data3_i    : std_logic_vector(4 - 1 downto 0);

    signal s_dp_i       : std_logic_vector(4 - 1 downto 0);
    signal s_dp_o       : std_logic;

    signal s_seg_o      : std_logic_vector(7 - 1 downto 0);
    signal s_dig_o      : std_logic_vector(4 - 1 downto 0);
begin
    -- Connecting testbench signals with driver_7seg_4digits entity
    -- (Unit Under Test)
    --- WRITE YOUR CODE HERE
    uut_driver_7seg : entity work.driver_7seg_4digits
    -----
    port map(
        clk      => s_clk_100MHz,
        reset    => s_reset,

        data0_i => s_data0_i,
        data1_i => s_data1_i,
        data2_i => s_data2_i,
        data3_i => s_data3_i,

        dp_i     => s_dp_i,

```

```
dp_o    => s_dp_o,  
seg_o   => s_seg_o,  
dig_o   => s_dig_o  
);
```

```
-----  
p_clk_gen : process  
begin  
    while now < 750 ns loop          -- 75 periods of 100MHz clock  
        s_clk_100MHz <= '0';  
        wait for c_CLK_100MHZ_PERIOD / 2;  
        s_clk_100MHz <= '1';  
        wait for c_CLK_100MHZ_PERIOD / 2;  
    end loop;  
    wait;  
end process p_clk_gen;
```

```
-----  
-- Reset generation process  
-----
```

```
--- WRITE YOUR CODE HERE
```

```
p_reset_gen : process  
begin  
    s_reset <= '0';  
    wait for 10 ns;  
  
    -- Reset activated  
    s_reset <= '1';  
    wait for 53 ns;  
  
    -- Reset deactivated  
    s_reset <= '0';  
  
    wait;  
end process p_reset_gen;
```


```
-----  
-- Data generation process  
-----
```

```
p_stimulus : process  
begin  
    report "Stimulus process started" severity note;
```

```
s_data3_i    <= "0011";
s_data2_i    <= "0001";
s_data1_i    <= "0100";
s_data0_i    <= "0010";
s_dp_i       <= "0111";

wait for 600 ns;
s_data3_i    <= "0000";
s_data2_i    <= "0001";
s_data1_i    <= "0000";
s_data0_i    <= "0001";

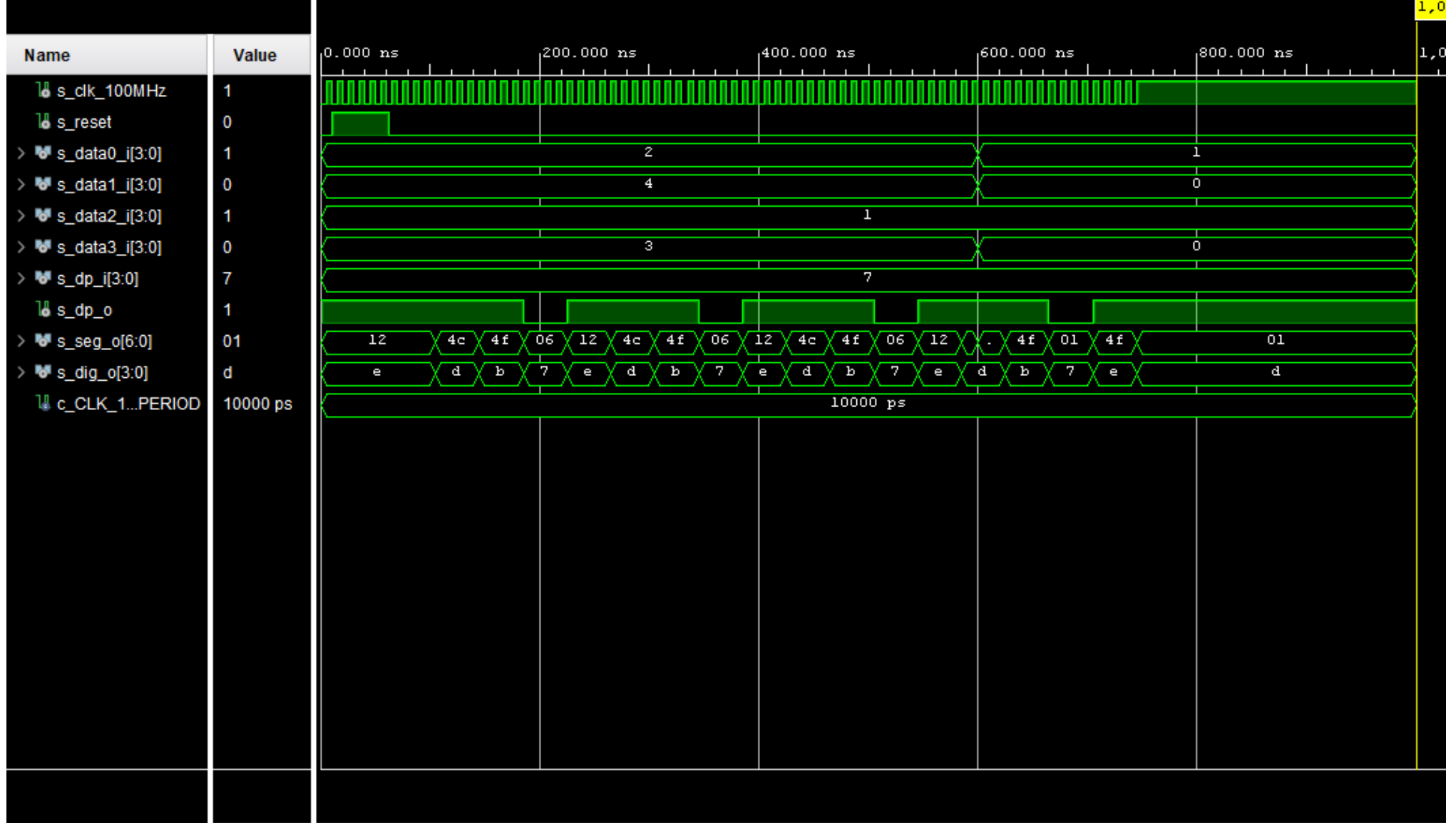report "Stimulus process finished" severity note;
wait;
end process p_stimulus;
end architecture testbench;
```



##Listing of VHDL architecture of the top layer.

```
architecture Behavioral of top is
    -- No internal signals
begin
```

```
-----
-- Instance (copy) of driver_7seg_4digits entity
driver_seg_4: entity work.driver_7seg_4digits
```

```

port map(
    clk          => CLK100MHZ,
    reset        => BTNC,
    data0_i(3)   => SW(3),
    data0_i(2)   => SW(2),
    data0_i(1)   => SW(1),
    data0_i(0)   => SW(0),
    --
    data1_i(3)   => SW(7),
    data1_i(2)   => SW(6),
    data1_i(1)   => SW(5),
    data1_i(0)   => SW(4),
    --
    data2_i(3)   => SW(11),
    data2_i(2)   => SW(10),
    data2_i(1)   => SW(9),
    data2_i(0)   => SW(8),
    --
    data3_i(3)   => SW(15),
    data3_i(2)   => SW(14),
    data3_i(1)   => SW(13),
    data3_i(0)   => SW(12),

    dig_o =>     AN(4-1 downto 0),

    seg_o(0)     => CA,
    seg_o(1)     => CB,
    seg_o(2)     => CC,
    seg_o(3)     => CD,
    seg_o(4)     => CE,
    seg_o(5)     => CF,
    seg_o(6)     => CG,

    dp_i => "0111",
    dp_o => DP
    --- WRITE YOUR CODE HERE
);

```

```

-- Disconnect the top four digits of the 7-segment display
AN(7 downto 4) <= b"1111";

```



## Eight-digit driver. Submit:

Image of the driver schematic. The image can be drawn on a computer or by hand.

