
 [xkocum00](#) Update README.md


Latest commit 102582a 2 minutes ago [History](#)

 1 contributor

Digital-electronics-1

Lab assignment 3)

Preparation tasks:

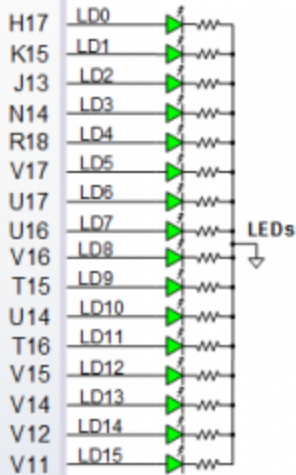

Hex	Inputs	A	B	C	D	E	F	G
-----	--------	---	---	---	---	---	---	---

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

2.Seven-segment display decoder

Architecture code (hex_7seg.vhd)

```
p_7seg_decoder : process(hex_i)
begin
```

```

case hex_i is
  when "0000" =>
    seg_o <= "0000001";    -- 0
  when "0001" =>
    seg_o <= "1001111";    -- 1
  when "0010" =>
    seg_o <= "0010010";    -- 2
  when "0011" =>
    seg_o <= "0000110";    -- 3
  when "0100" =>
    seg_o <= "1001100";    -- 4
  when "0101" =>
    seg_o <= "0100100";    -- 5
  when "0110" =>
    seg_o <= "0100000";    -- 6
  when "0111" =>
    seg_o <= "0001111";    -- 7
  when "1000" =>
    seg_o <= "0000000";    -- 8
  when "1001" =>
    seg_o <= "0000100";    -- 9
  when "1010" =>
    seg_o <= "0001000";    -- A
  when "1011" =>
    seg_o <= "1100000";    -- B
  when "1100" =>
    seg_o <= "0110001";    -- C
  when "1101" =>
    seg_o <= "1000010";    -- D
  when "1110" =>
    seg_o <= "0110000";    -- E
  when others =>
    seg_o <= "0111000";    -- F
end case;
end process p_7seg_decoder;

```

Testbench code (tb_hex_7seg.vhd)

```

p_stimulus : process
begin
  -- Report a note at the begining of stimulus process

```

```

report "Stimulus process started. -----" severity note;

s_hex <= "0000";    wait for 10 ns;    -- 0

s_hex <= "0001";    wait for 10 ns;    -- 1

s_hex <= "0010";    wait for 10 ns;    -- 2

s_hex <= "0011";    wait for 10 ns;    -- 3

s_hex <= "0100";    wait for 10 ns;    -- 4

s_hex <= "0101";    wait for 10 ns;    -- 5

s_hex <= "0110";    wait for 10 ns;    -- 6

s_hex <= "0111";    wait for 10 ns;    -- 7

s_hex <= "1000";    wait for 10 ns;    -- 8

s_hex <= "1001";    wait for 10 ns;    -- 9

s_hex <= "1010";    wait for 10 ns;    -- A

s_hex <= "1011";    wait for 10 ns;    -- B

s_hex <= "1100";    wait for 10 ns;    -- C

s_hex <= "1101";    wait for 10 ns;    -- D


s_hex <= "1110";    wait for 10 ns;    -- E

s_hex <= "1111";    wait for 10 ns;    -- F

    report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Simulated waveform

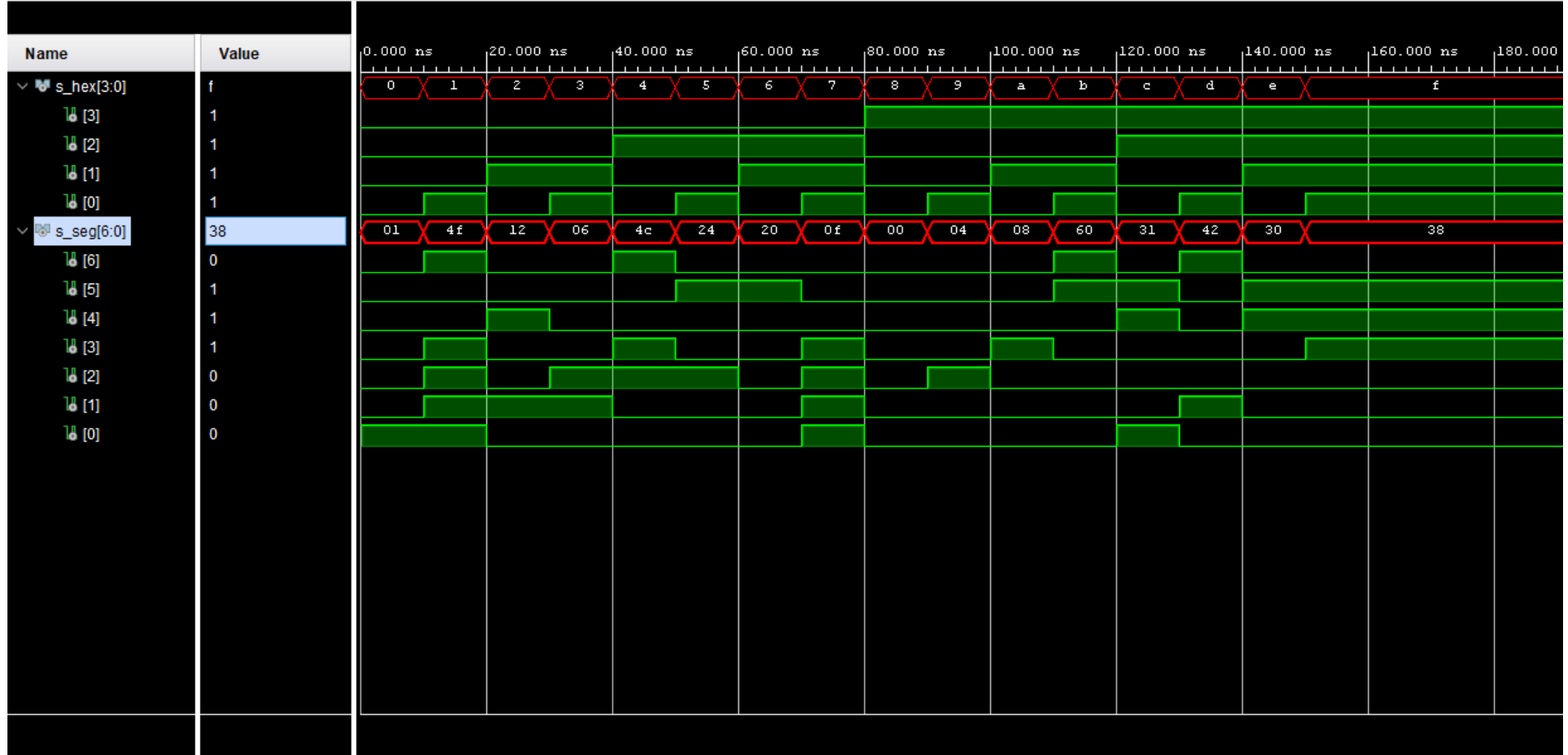

Top 7-segment module instantiation (top.vhd)

```
-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
    port map(
        hex_i      => SW,
        seg_o(6)   => CA,
        seg_o(5)   => CB,
        seg_o(4)   => CC,
        seg_o(3)   => CD,
        seg_o(2)   => CE,
        seg_o(1)   => CF,
        seg_o(0)   => CG
    );
```

Part 3: LED(7:4) indicators

LED[7:4] truth table

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity top is
    Port (
        SW  : in  std_logic_vector(4 - 1 downto 0);
        LED : out std_logic_vector(16 - 1 downto 0);

        CA  : out std_logic;
        CB  : out std_logic;
        CC  : out std_logic;
        CD  : out std_logic;
        CE  : out std_logic;
        CF  : out std_logic;
        CG  : out std_logic;

        AN  : out std_logic_vector(8 - 1 downto 0)
    );
end top;

architecture Behavioral of top is
    signal s_seg_o : std_logic_vector(7 - 1 downto 0);
begin
    -- Instance (copy) of hex_7seg entity
```

```

hex2seg : entity work.hex_7seg
    port map(
        hex_i      => SW,
        seg_o      => s_seg_o
    );

-- Connect one common anode to 3.3V
AN <= b"1111_1110";

CA <= s_seg_o(6);
CB <= s_seg_o(5);
CC <= s_seg_o(4);
CD <= s_seg_o(3);
CE <= s_seg_o(2);
CF <= s_seg_o(1);
CG <= s_seg_o(0);

LED(15 downto 9) <= not s_seg_o;

-- Display input value LED
LED(3 downto 0) <= SW;

-- Turn LED(4) on if input value is equal to 0, ie "0000"
LED(4) <= '1' when (SW = "0000") else '0';

-- Turn LED(5) on if input value is greater than 9
LED(5) <= '1' when (unsigned(SW) > 9) else '0';

-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
LED(6) <= '1' when (unsigned(SW) mod 2 = 1) else '0';

-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
LED(7) <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or SW = "1000") else '0';

end Behavioral;

```

Hex	Inputs	LED[7]	LED[6]	LED[5]	LED[4]
0	0000	0	0	0	1
1	0001	1	1	0	0

Hex	Inputs	LED[7]	LED[6]	LED[5]	LED[4]
2	0010	1	0	1	0
3	0011	0	1	0	0
4	0100	1	0	0	0
5	0101	0	1	0	0
6	0110	0	0	0	0
7	0111	0	1	0	0
8	1000	1	0	0	0
9	1001	0	1	0	0
A	1010	0	0	1	0
b	1011	0	1	1	0
C	1100	0	0	1	0
d	1101	0	1	1	0
E	1110	0	0	1	0
F	1111	0	1	1	0